



Prepared by:

WD8PU



The Holla

Amateur
Radio Club

A Course
for Technicians

and
General
S

Circuits

Beyond knowing these schematic images, the amateur must also know that a good conductor is metals such as...

- Copper
- Gold
- Silver
- Aluminum

An insulator of electricity is non metallic...


- Glass
- Air

NOTE: an "Open Circuit" can have no current, a "Short Circuit" has too much


Schematics



CHASSIS
GROUND

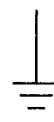

EARTH
GROUND

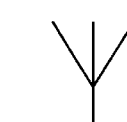


ANTENNA




VARIABLE
RESISTOR




FIXED
RESISTOR

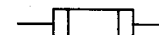

FUSE

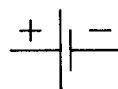


SINGLE-CELL
BATTERY

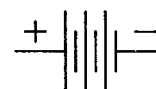


MULTIPLE-CELL
BATTERY




SINGLE-POLE,
SINGLE-THROW
SWITCH

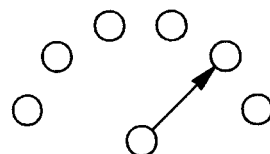

SINGLE-POLE,
6 POSITION
ROTARY SWITCH

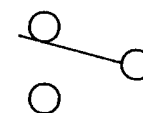

SINGLE-POLE,
DOUBLE-THROW
SWITCH

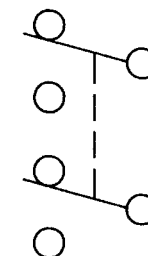

DOUBLE-POLE,
DOUBLE-THROW
SWITCH



Prepared by:

WD8PU

**The
Holla**
Amateur
Radio Club
A Course
for Technicians
and
General
Operators

- All chassis grounds in RF equipment ought to be earth grounded by means of a “daisy chain” connection of equipment to a single earth ground.
- The earth ground ought to be a 8’ copper rod in the ground as an absolute minimum...underground wire radials emanating from the copper ground rod will help considerably.
- Never use multiple grounds. A good ground will reduce atmospheric noise into your receiver, and improve transmitter performance.
- When antennas are not in use, always ground both coax conductors. During thunder storms, disconnect the ground, power cords, and all antenna connections from your equipment. Even a close lightning strike can destroy your solid state radios.
- Poor equipment grounding can increase the likelihood that your station will cause Radio Frequency Interference (TVI) (RFI).
- A poor equipment ground can result in electrical shock and even RF burns.
- The “green-wire” in a three-wire AC line cord power supply ought to be connected to the chassis ground.
- Grounding helps minimize “audio rectification” (by



Prepared by:

WD8PU




The Holla
Amateur
Radio Club
A Course
for Technicians
and
General
S


While transistors can serve in many different electronic applications, they are commonly used for low-voltage amplifier circuits.

An oscillator is similar to an amplifier circuit with some of the output fed back into the input to cause an oscillation at a certain frequency.


Triode vacuum tubes operate commonly as high

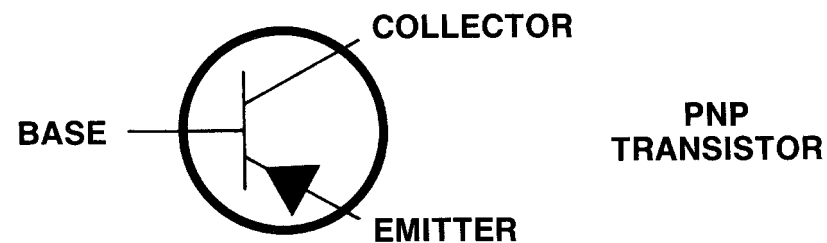

Pointing IN
Pointer


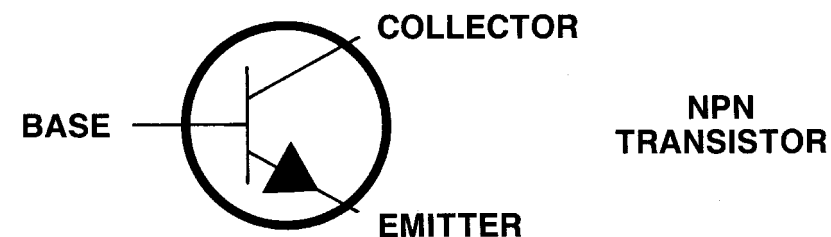


Not
Pointing IN

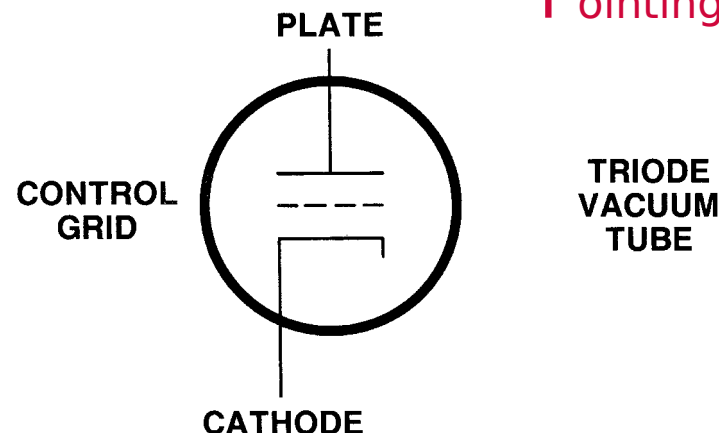



Schematics... Low Pass Filter

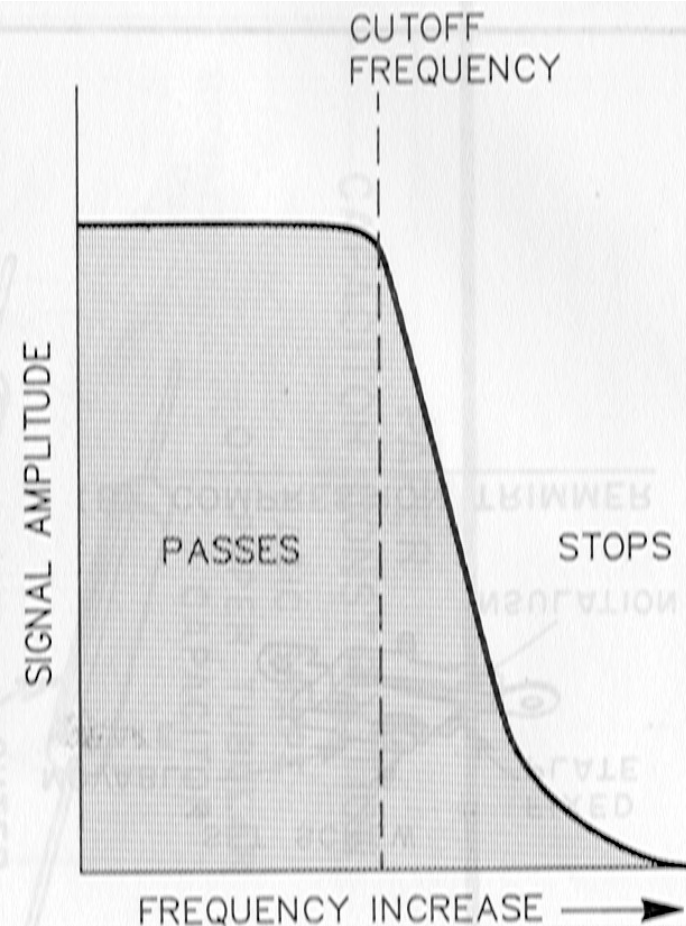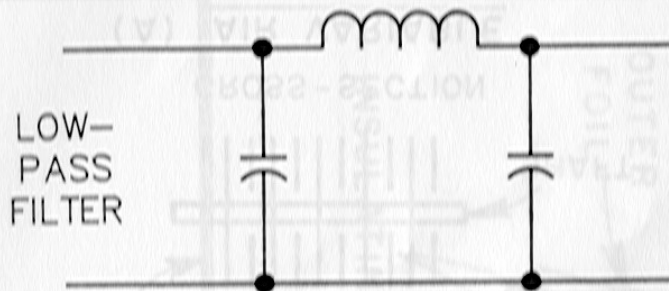

A Low Pass filter is used in the output of transmitters to eliminate harmonic radiation (Unwanted multiples of the transmitting frequency) that may cause RFI (Radio frequency Interference).

Prepared by:

WD8PU



The Holla


Amateur
Radio Club

A Course
for Technicians


and
General
S



Schematics...

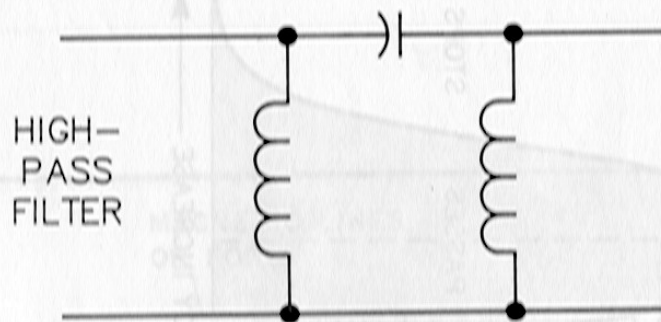

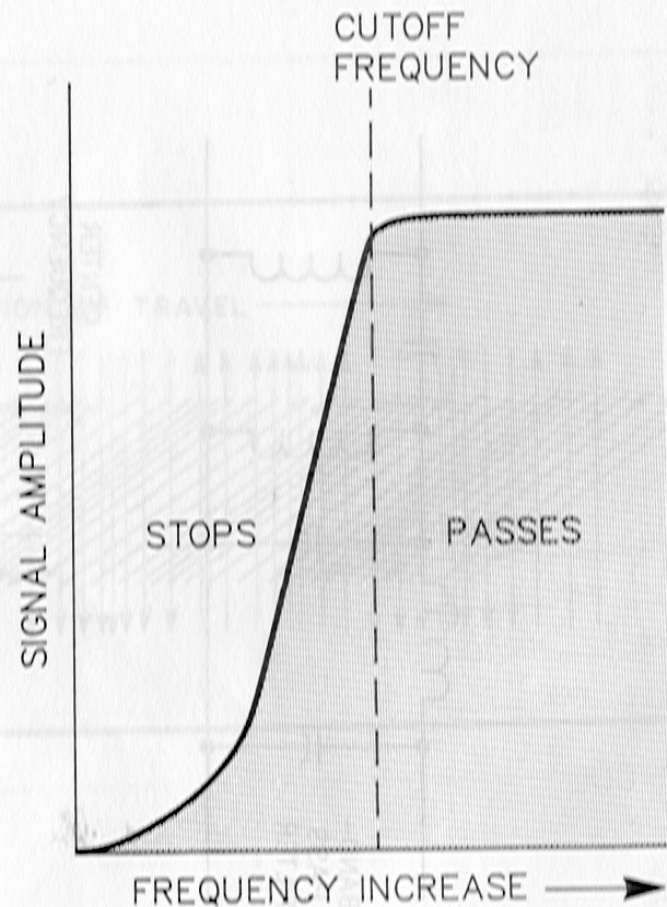High Pass Filters are often used at a receiver's "front-end" to help eliminate interference caused from receiver overload of a transmitter on a lower frequency. A good example would be TVI (Television Interference). A typical Amateur station producing TVI is operating below 30 MHz. A High Pass Filter placed at the antenna input of the TV, and set for 54



NOTE: The radio operator is always responsible for correcting TVI caused by harmonic radiation. Overload is the

Prepared by:


WD8PU



The Holla
Amateur
Radio Club
A Course
for Technicians
and
General
Operators




Schematics...

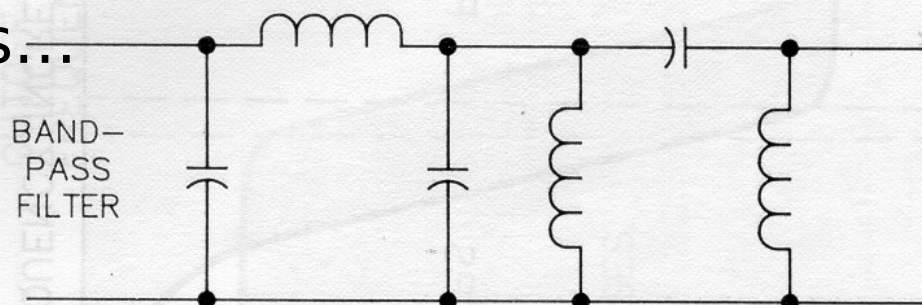

Band Pass Filters are a combination of both Low Pass and High Pass filters. The result is a sharp frequency pass curve.

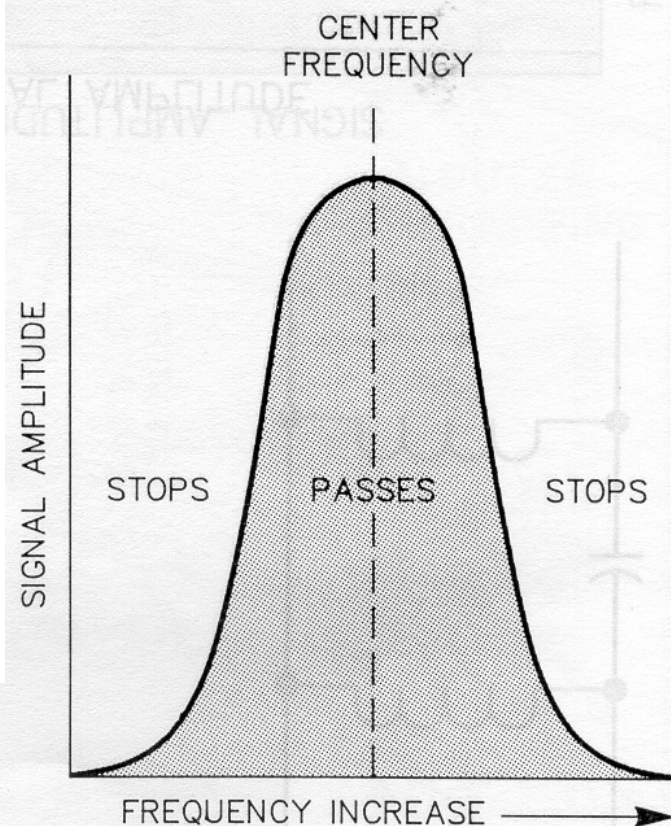Band Pass Filters are used in the IF (Intermediate Frequency) section of receivers to block energy outside a certain frequency range.



Prepared by:
WD8PU



The Holla
Amateur
Radio Club
A Course
for Technicians
and
General
Operators



Prepared by:

WD8PU



**The
Holla**

**Amateur
Radio Club**

**A Course
for Technicians
and
General
S**

Wiring Code

- Residential electrical 120 volt cable contains a White (hot) a black (hot) and typically a ground wire (bare).
- Residential electrical 240 volt cable contains a black (hot), a red (hot), a white (neutral) and a ground (bare).
- On a 240 volt power supply, overload fuses would be place on the hot leads (red & black).
- A 15 amp, 120 volt household circuit uses #14 gauge wire.
- A 20 amp, 120 volt household circuit uses #12 gauge wire.
- The maximum allowable circuit breaker to be used on a #12 gauge, 120 volt, household circuit is 20 Amps.
- The maximum allowable circuit breaker to be used on a #14 gauge, 120 volt household circuit is 15 Amps.

Ham Radio Basic Electronics: *Power Supplies* Lesson 6



Prepared by:

WD8PU



**The
Holla**
Amateur
Radio Club
A Course
for Technicians
and
General
Operators

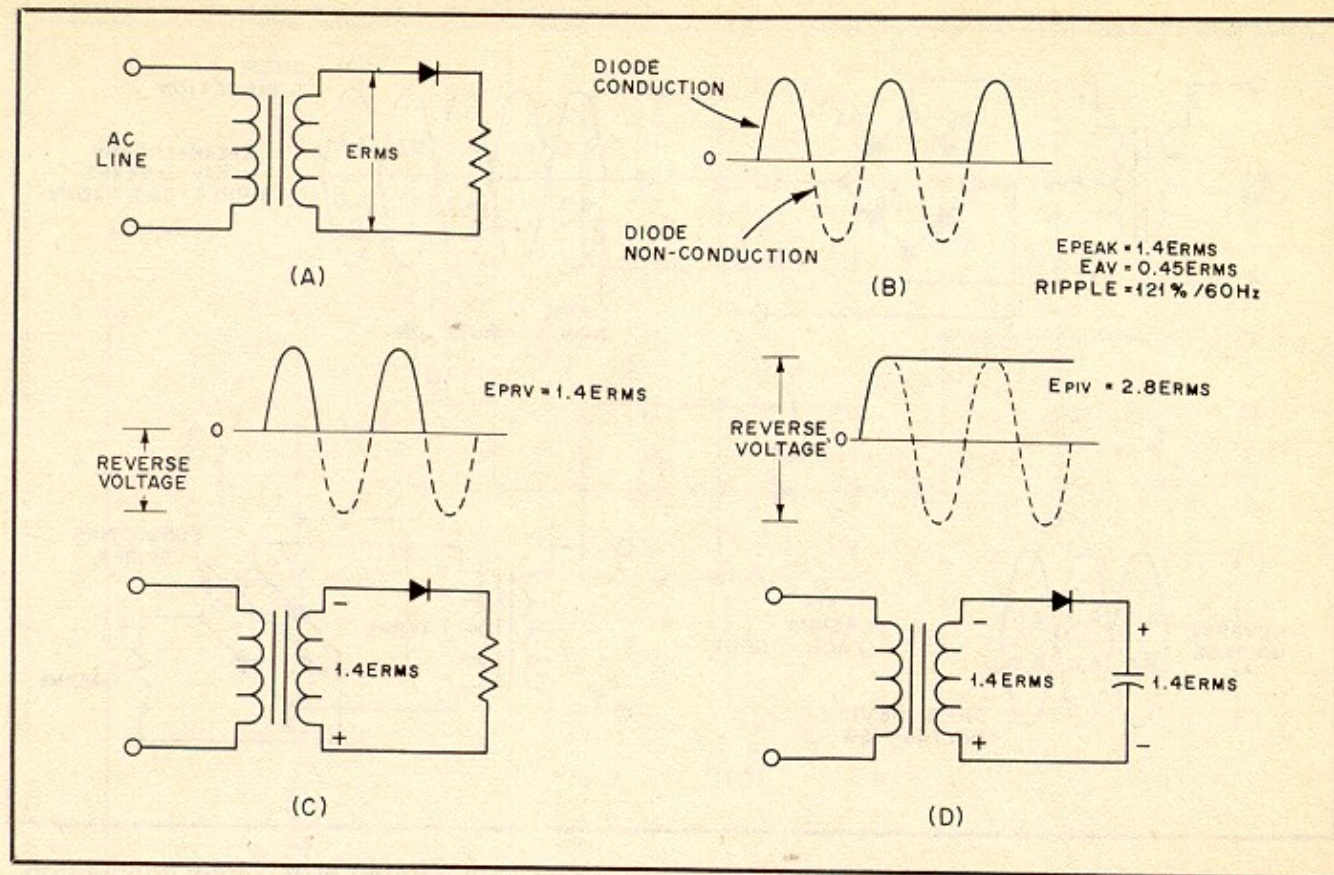


Fig. 5 — Half-wave rectifier circuit. A illustrates the basic circuit, and B displays the diode conduction and nonconduction periods. The peak-inverse voltage impressed across the diode is shown at C and D with a simple resistor load at C and a capacitor load at D. E_{PIV} is $1.4 E_{RMS}$ for the resistor load and $2.8 E_{RMS}$ for the capacitor load.

Note: the transformer winding ratio, the purpose of a diode, half-wave and full-wave rectification, capacitive & inductive filtering, bleed resistors.

Ham Radio Basic Electronics: *Power Supplies* Lesson 6



Prepared by:

WD8PU



**The
Holla**
Amateur
Radio Club
A Course
for Technicians
and
General
Operators

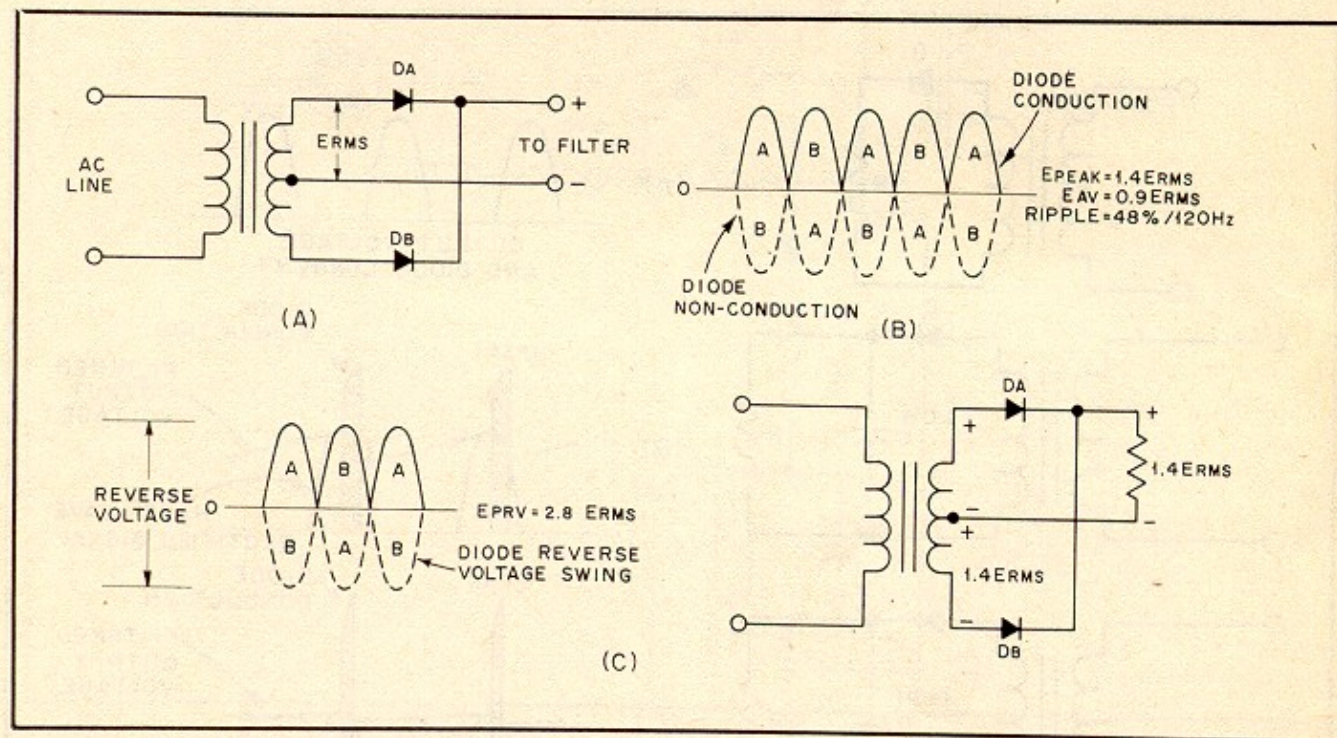


Fig. 6 — Full-wave center-tap rectifier circuit. A illustrates the basic circuit. Diode conduction is shown at B with diodes A and B alternately conducting. The peak-inverse voltage for each diode is $2.8 E_{RMS}$ as depicted at C.

Ham Radio Basic Electronics: *Power Supplies* Lesson 6



Prepared by:

WD8PU



**The
Holla**
Amateur
Radio Club
A Course
for Technicians
and
General
S

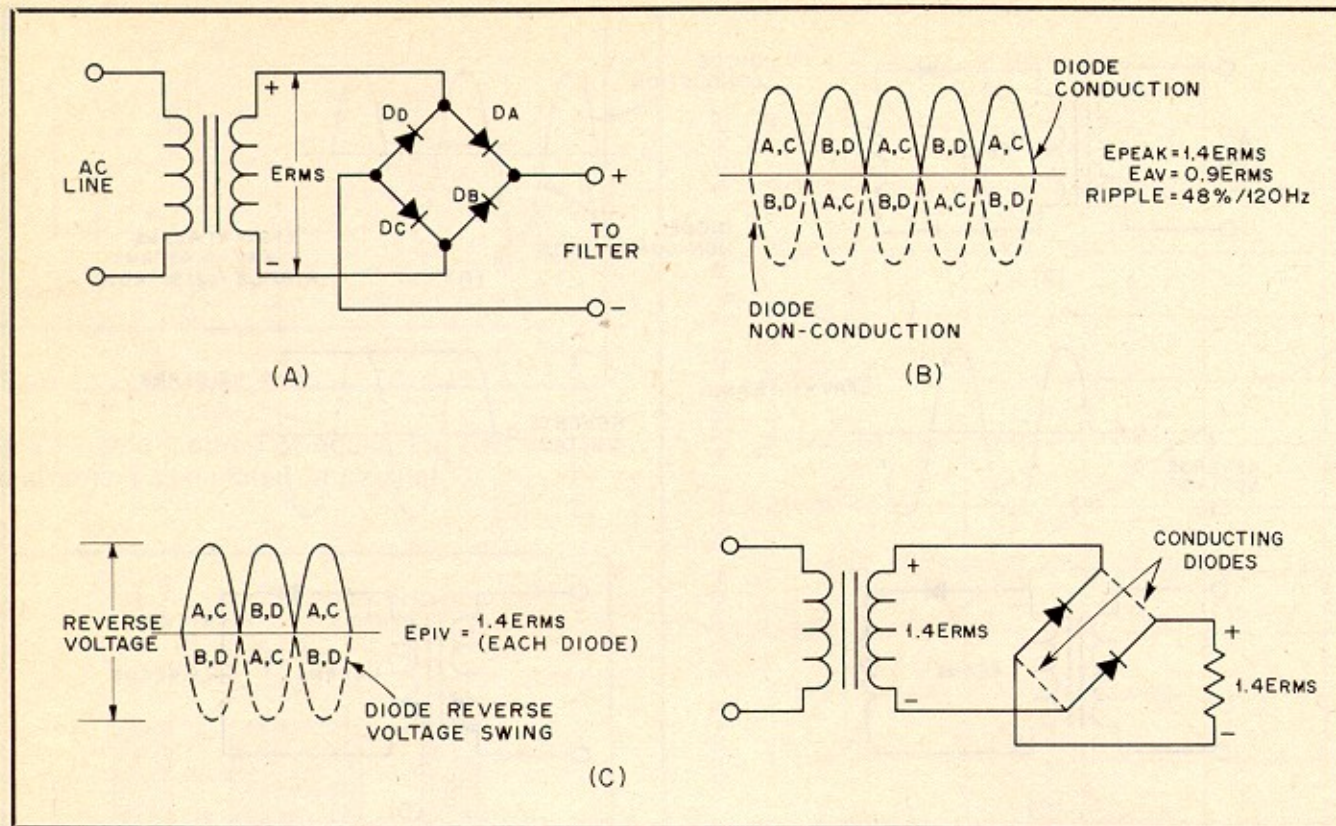


Fig. 7 — Full-wave bridge rectifier circuit. The basic circuit is illustrated at A. Diode conduction and nonconduction times are shown at B. Diodes A and C conduct on one half of the input cycle while diodes B and D conduct on the other. C displays the peak inverse voltage for one-half cycle. Since this circuit reverse-biases two diodes essentially in parallel, $1.4 E_{RMS}$ is applied across each diode.

*Inverse voltage rating of the diodes ought to be double of the output voltage of the power supply.

Ham Radio Basic Electronics: *Power Supplies* Lesson 6



Prepared by:

WD8PU



**The
Holla**
Amateur
Radio Club
A Course
for Technicians
and
General
S

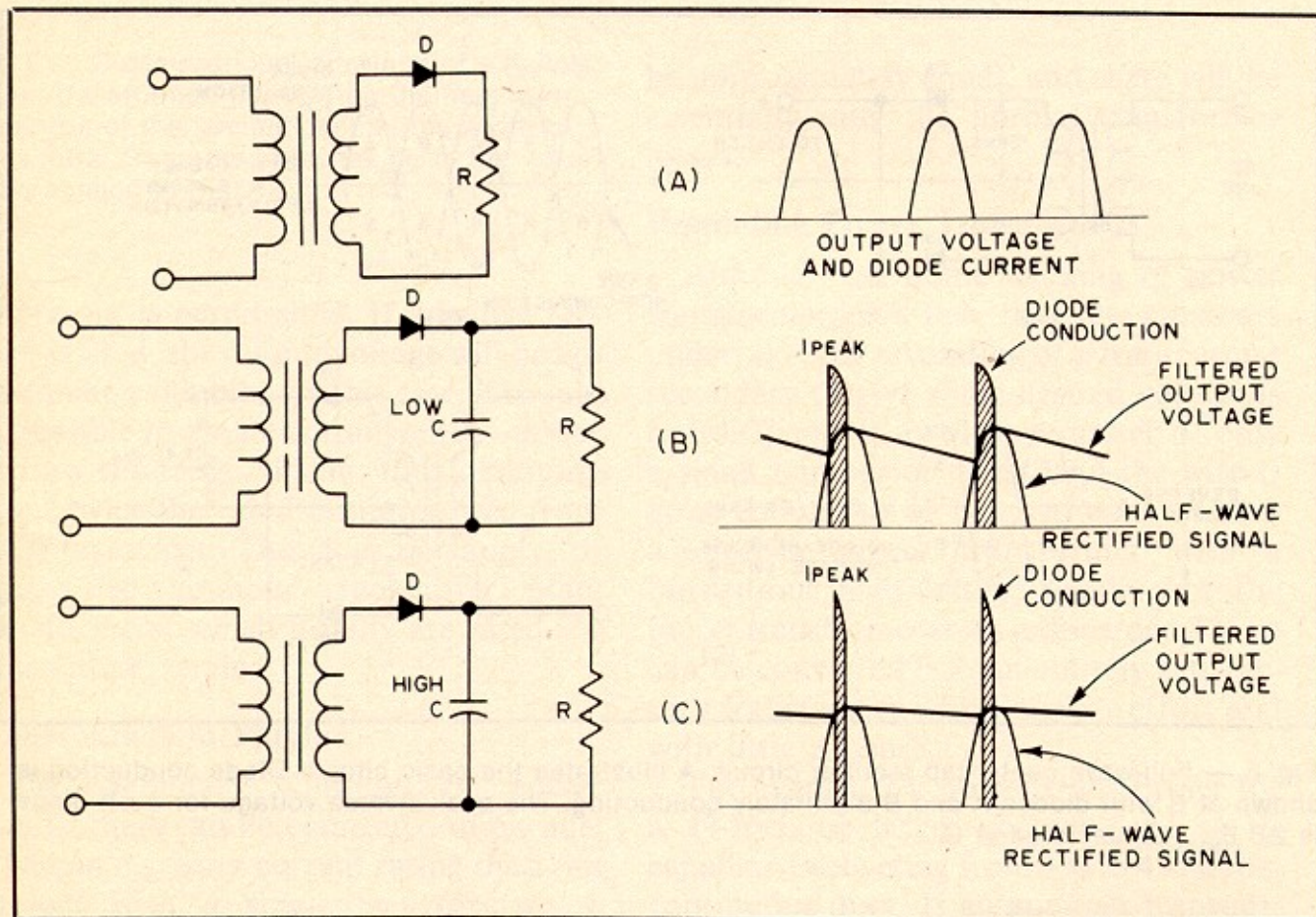


Fig. 8 — The circuit shown at A is a simple half-wave rectifier with a resistive load. The waveform shown to the right is that of output voltage and diode current. B illustrates how the diode current is modified by the addition of a capacitor filter. The diode conducts only when the rectified voltage is greater than stored capacitor voltage. Since this time period is usually only a short portion of a cycle, the peak current will be quite high. C shows an even higher peak current. This is caused by the larger capacitor, which effectively shortens the conduction period of the diode.

Ham Radio Basic Electronics: *Power Supplies* Lesson 6



Prepared by:

WD8PU



The Holla
Amateur
Radio Club
A Course
for Technicians
and
General
Operators

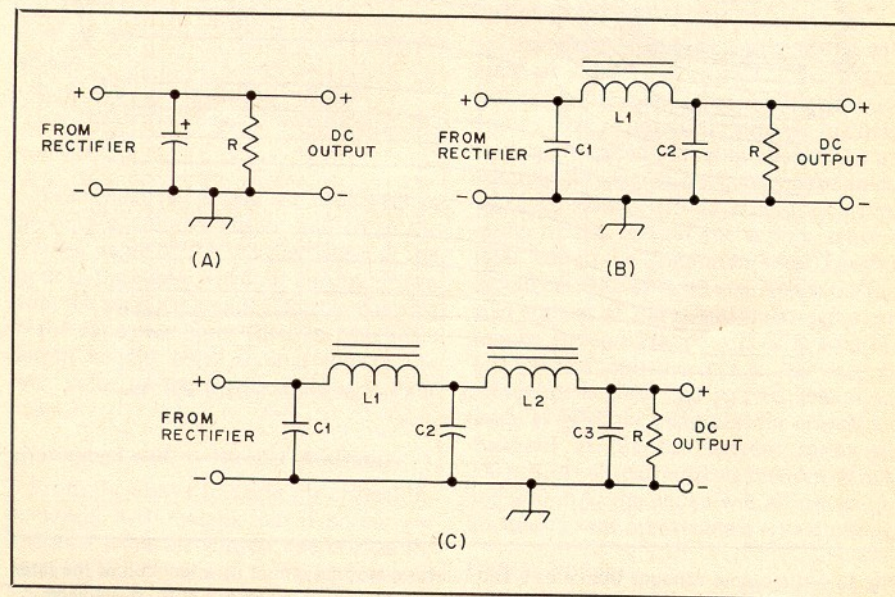


Fig. 12 — Capacitor-input filter circuits. At A is a simple capacitor filter. B and C are single- and double-section filters, respectively.

- Diodes connected in series should be shunted with equalizing resistors and spike-protecting capacitors.

- Diodes connected in parallel should have series current equalizing resistors.

- Capacitors in power supplies are always electrolytic which have a (+) and (-) pole.

- The inductor is considered a “choke” and resists the flow of AC while allowing the DC to pass.

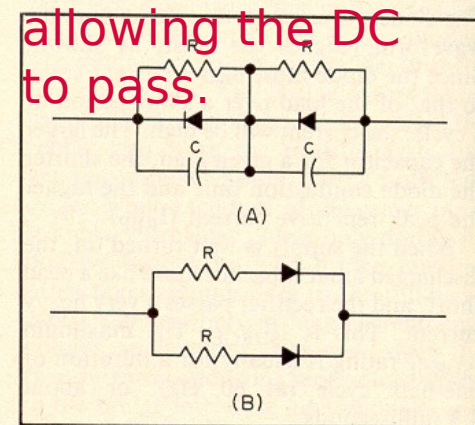


Fig. 11 — (A) Diodes connected in series should be shunted with equalizing resistors and spike-suppressing capacitors. (B) Diodes connected in parallel should have series current equalizing resistors.



Tutorial

The time dependence of alternating current raises questions about defining and measuring values of voltage, current and power. Because these parameters change from one instant to the next, one might wonder, for example, which point on the cycle characterizes the voltage or current for the entire cycle. A pure sine-wave reflects a total vertical displacement of "Peak-to-Peak" voltage.

When an AC voltage is applied to a resistor, the resistor will dissipate energy in the form of heat, just as if the voltage were DC. The DC voltage that would cause identical heating is the "root-mean-square" (RMS) voltage. Calculate by...

$$V_{\text{peak}} = V_{\text{RMS}} \times \sqrt{2} \approx V_{\text{RMS}} \times 1.414$$

$$V_{\text{RMS}} = \frac{V_{\text{peak}}}{\sqrt{2}} \approx V_{\text{peak}} \times 0.707$$

AC voltage is always expressed in terms of its RMS value (i.e., 117 volts RMS in your household outlet).

An electro-dynamic meter movement responds to the average value. Average household voltage is 105.2 volts. Calculate by...

$$V_{\text{peak}} = \frac{V_{\text{avg}}}{0.636} = V_{\text{avg}} \times 1.572$$

Prepared by:

WD8PU



The Holla

Amateur
Radio Club

A Course
for Technicians
and General
Operators



Prepared by:

WD8PU



The Holla
Amateur
Radio Club
A Course
for Technicians
and
General
S

Tutorial

RMS voltage x RMS current
= average power. The
average power used to heat
a resistor is equal to the DC
power required to produce
the same heat. Peak
voltage x peak current = 2
x average power.

In the context of radio
signals where a sine wave
is being modulated by a
voice, peak power means
maximum average power.
“Peak Envelope Power”
(PEP) is the parameter most
often used to express the
maximum signal-handling
capability of a linear power
amplifier. To compute the
PEP of a waveform, multiply
the PEV by .707 to obtain
the RMS value, square the

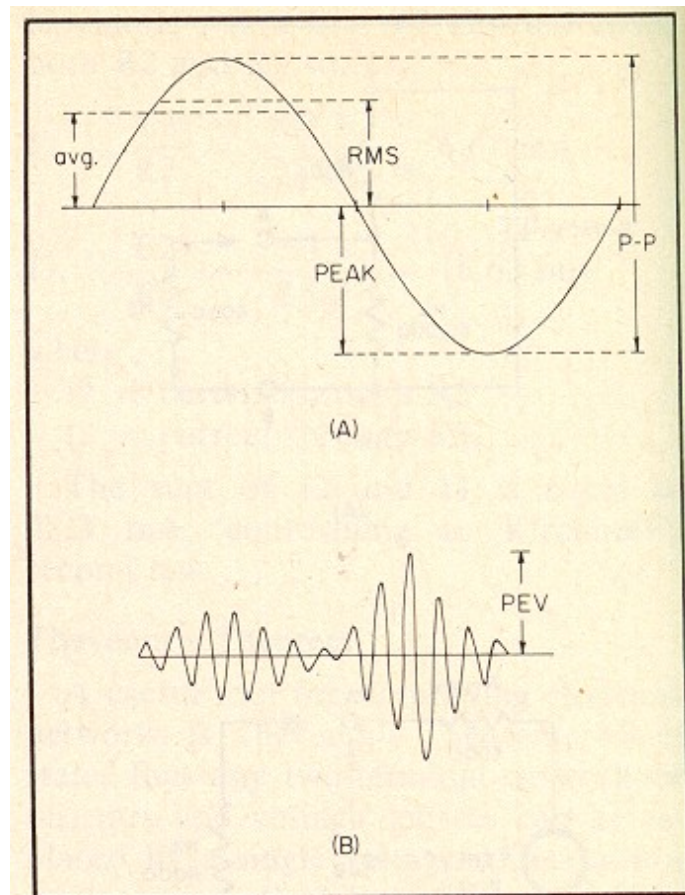


Fig. 21 — Ac voltage and current measurements. The sine-wave parameters are illustrated at A, while B shows the peak envelope voltage (PEV) for a composite waveform.

Ham Radio Basic Electronics: AC Power Tutorial



Prepared by:

WD8PU



**The
Holla**
Amateur
Radio Club
*A Course
for Technicians
and
General
S*

End of Lesson 6